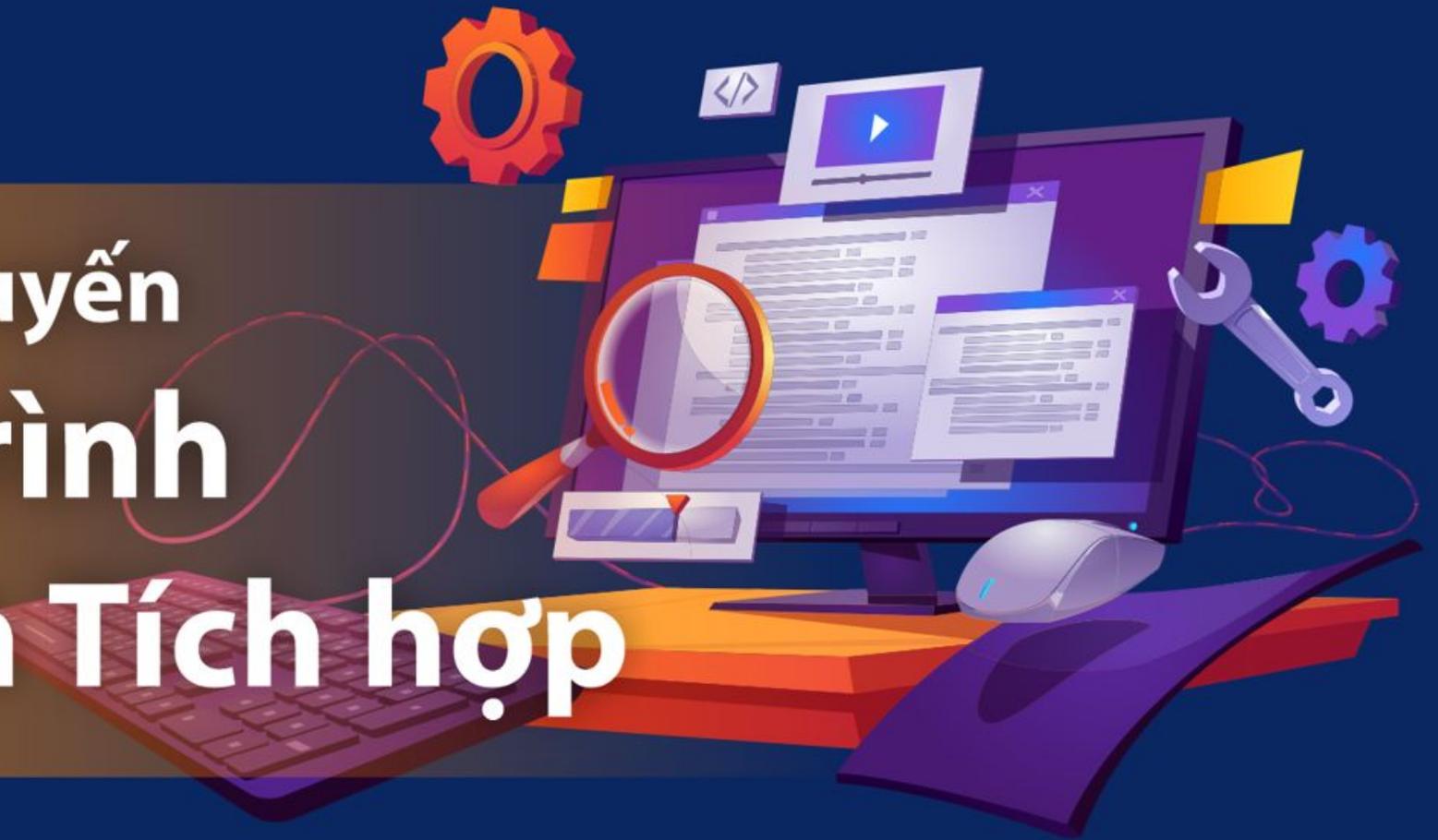



Lớp học Trực tuyến  
Chương trình  
Tiếng Anh Tích hợp


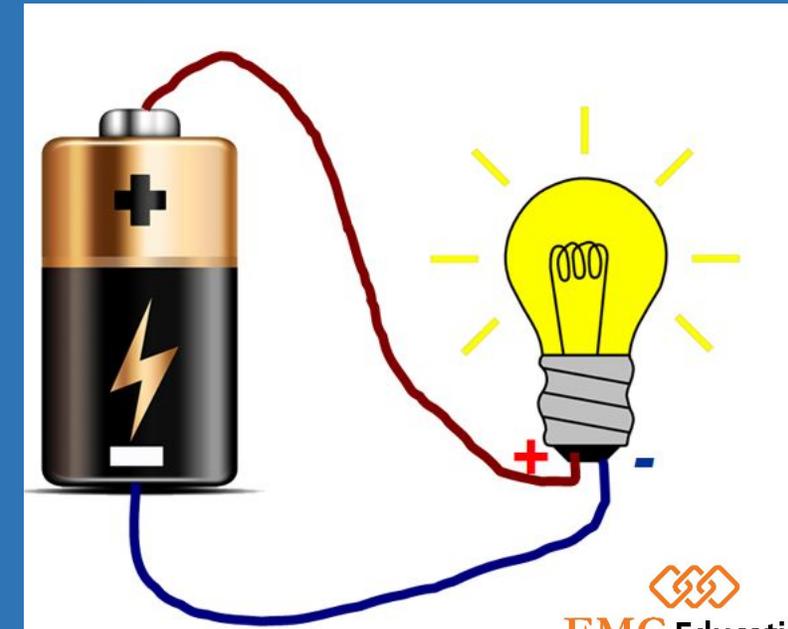
# Today's lesson: Circuits




- Parts of a circuit
- Component functions
- Circuit symbols
- Drawing circuits



# Things to remember


a  
complete  
circuit

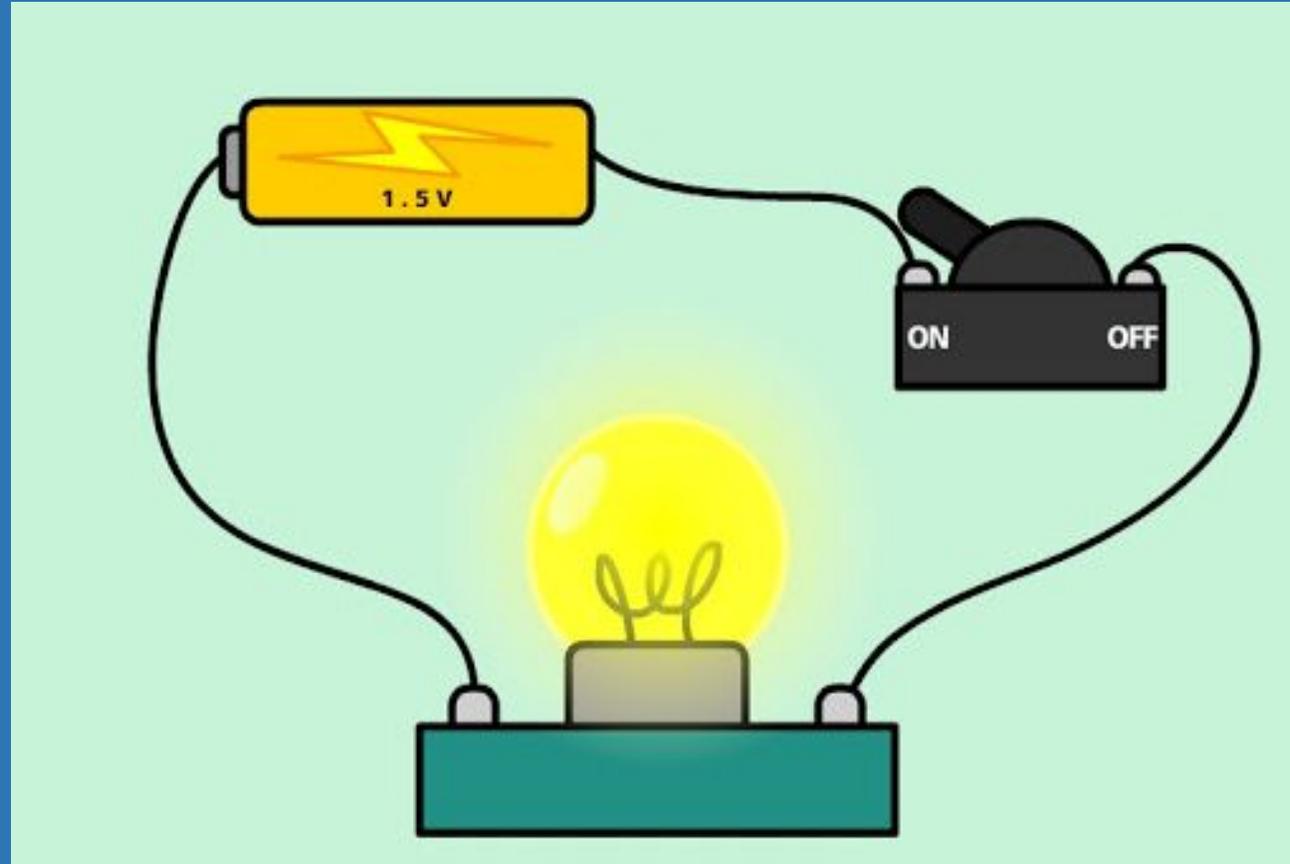

Electricity flows through the circuit.

# Things to remember



**an  
incomplete  
circuit**

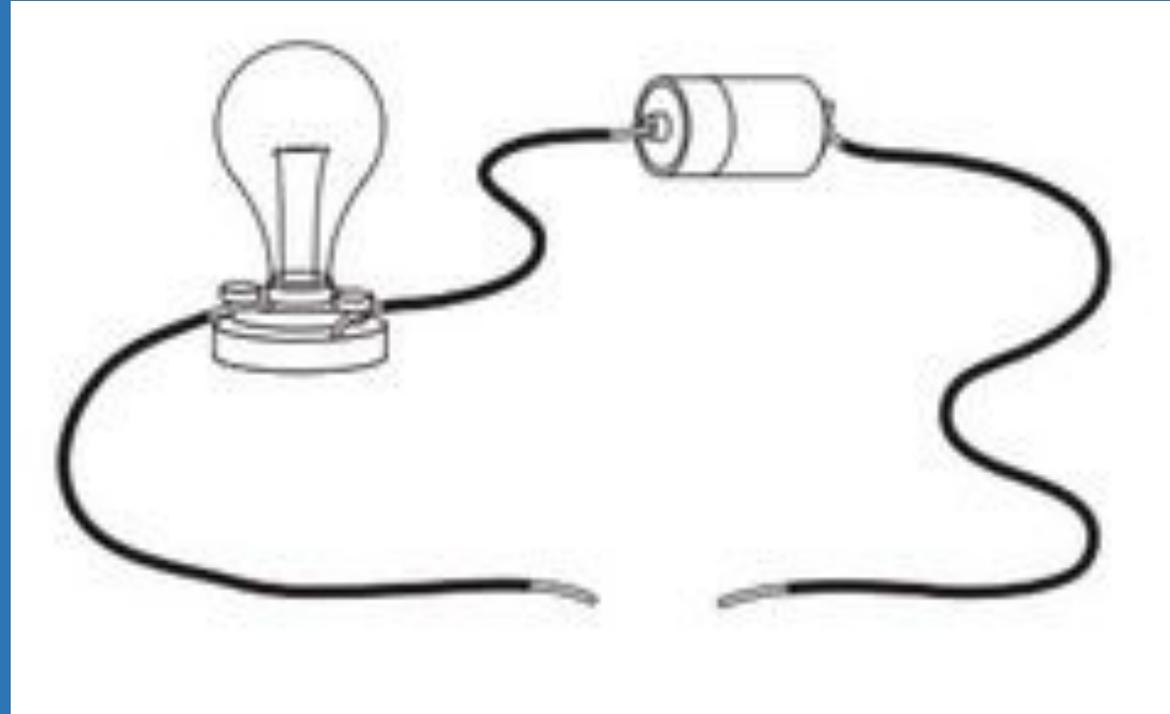


**The circuit  
is broken.**


Electricity can't flow - the light doesn't work.

# Components (the parts of a circuit)

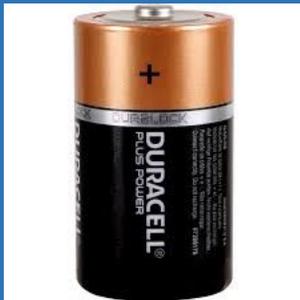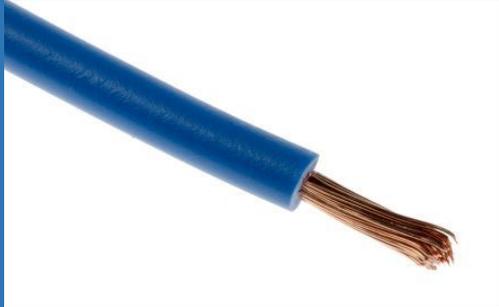


Make sure you take some notes!

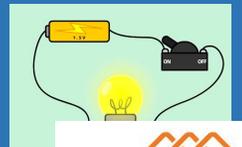

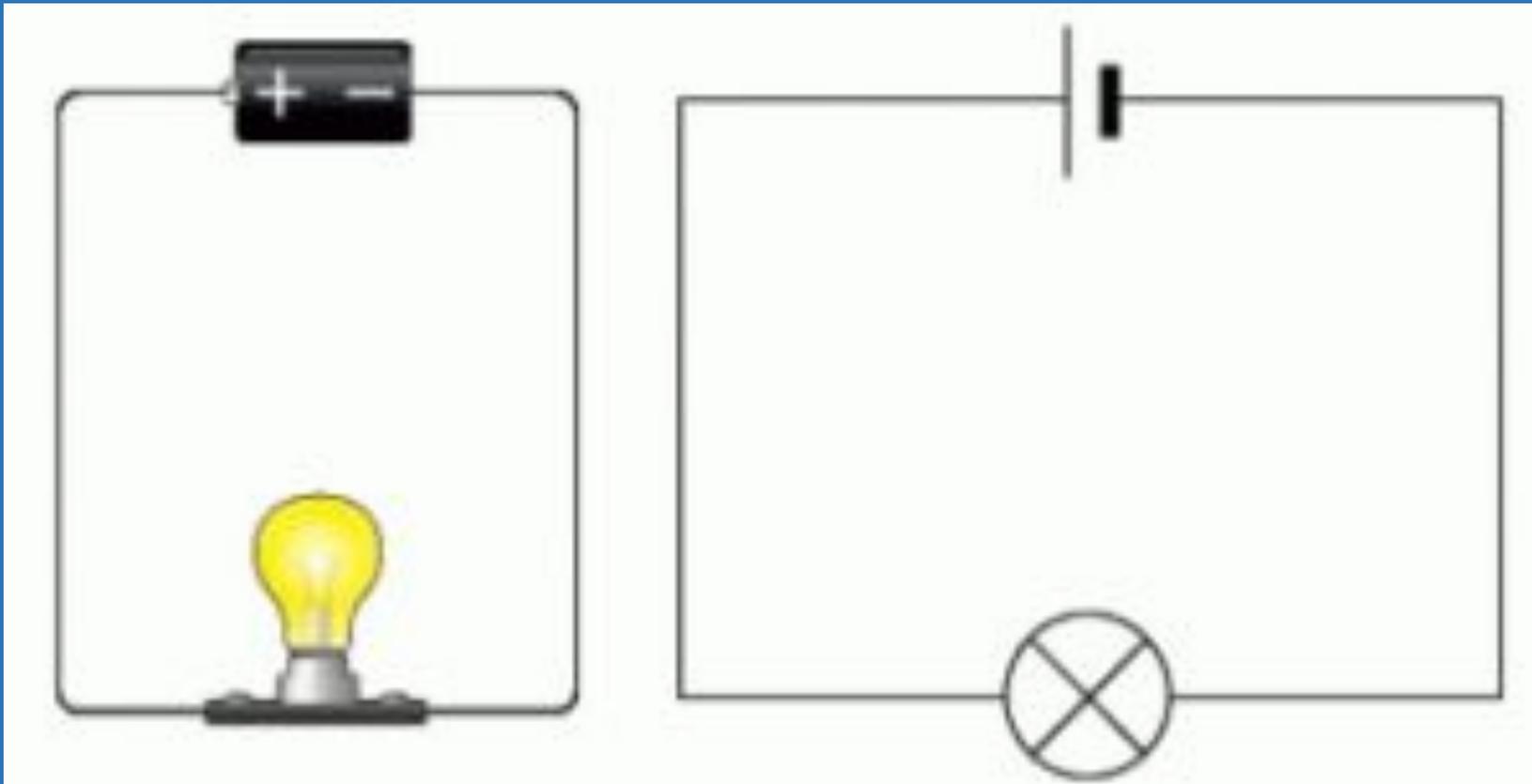


Circuits have many **components** that work together to make something light up, move or make a sound.

# What is it?

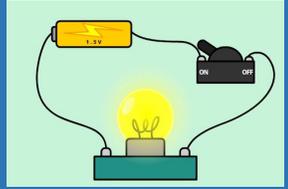


# What is it?

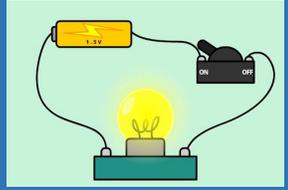


a battery  
or  
a cell


# What does it do? (function)

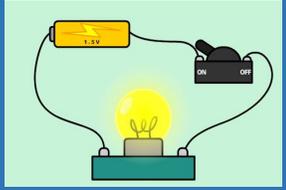

# What does it do? (function)

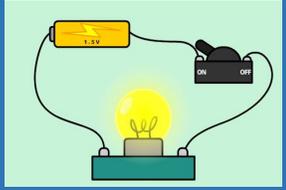


It gives energy  
to the circuit.

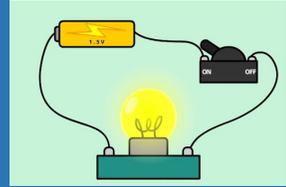


**There are many types of cell!**  
**Where do these come from?**

# What is it?

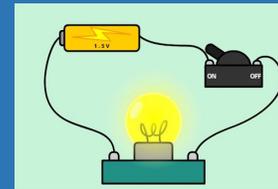


# What is it?

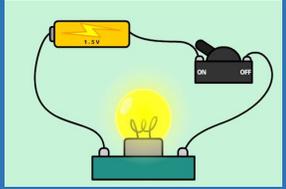


a light  
a lamp  
a bulb

# What does it do? (function)

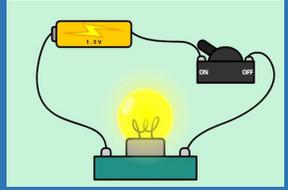


# What does it do? (function)

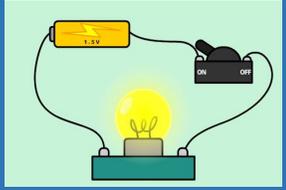


It makes a  
light!



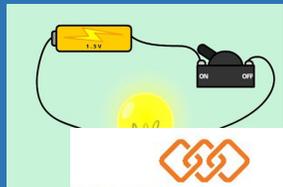
**There are lights everywhere!**  
**We studied about light in term 1!**



# What is it?

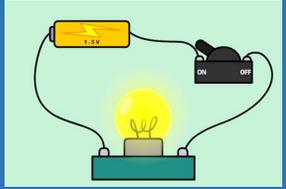


# What is it?

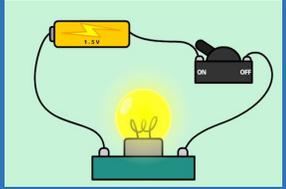


a switch

# What does it do?

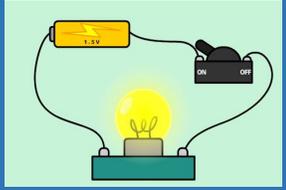

# What does it do?

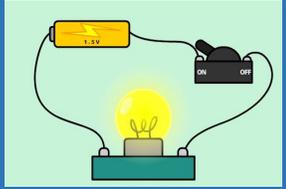

It completes and breaks a circuit.



Can you see any switches near you?

# What is it?



# What is it?



**a motor**


# What is its function?



**a motor**




# What is its function?

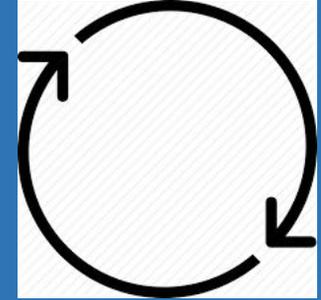

**It makes a  
shaft spin.**

# What is its function?

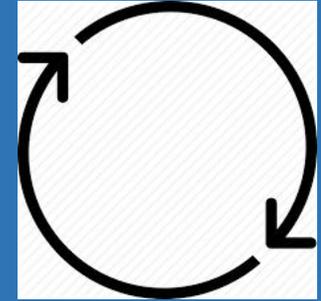

Can you think  
of anything  
that uses a  
motor?





fan



electric car



blender

These all use motors.

# What is it?



# What is it?



a buzzer


# What is its function?


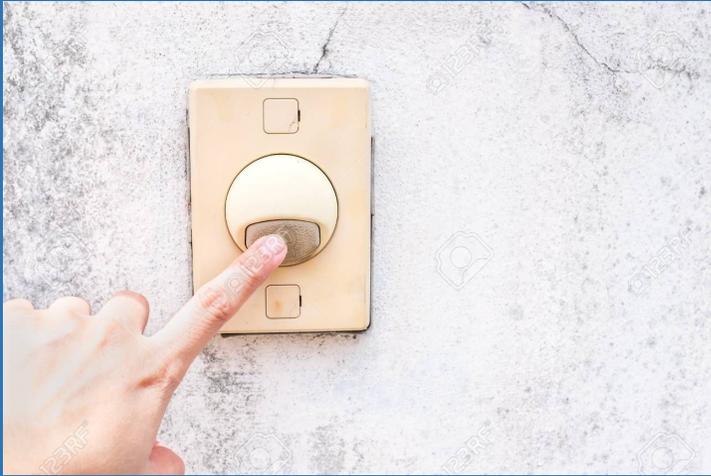
# What is its function?



It makes a  
sound.  
Bzzzzzzzzzzzz  
zz!!!!!!!!!!!!




**door buzzer**

Can you think of anything else that has a buzzer inside?




**alarm  
clocks**

# What is it?

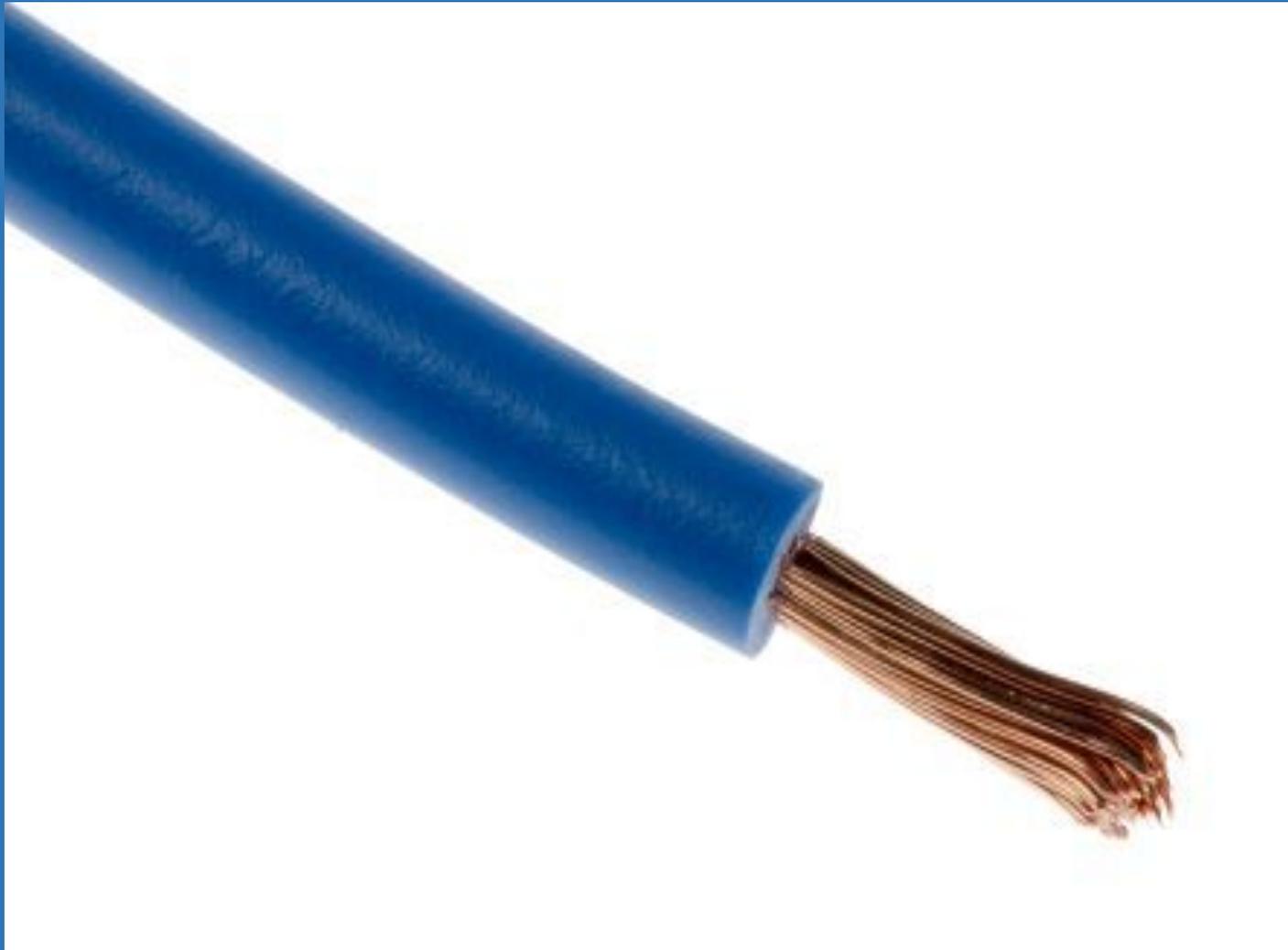


# What is it?

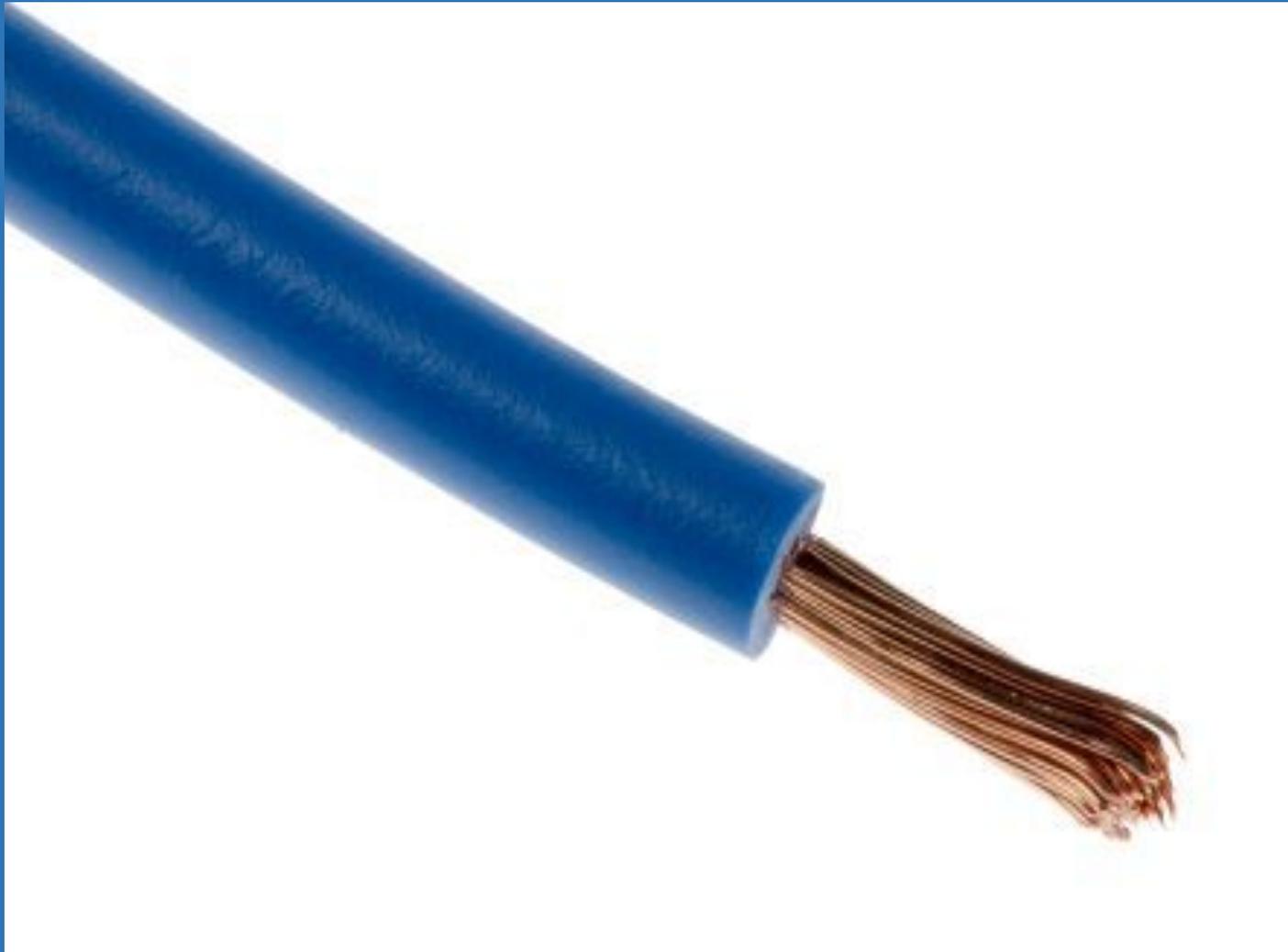


a wire

# What is its function?



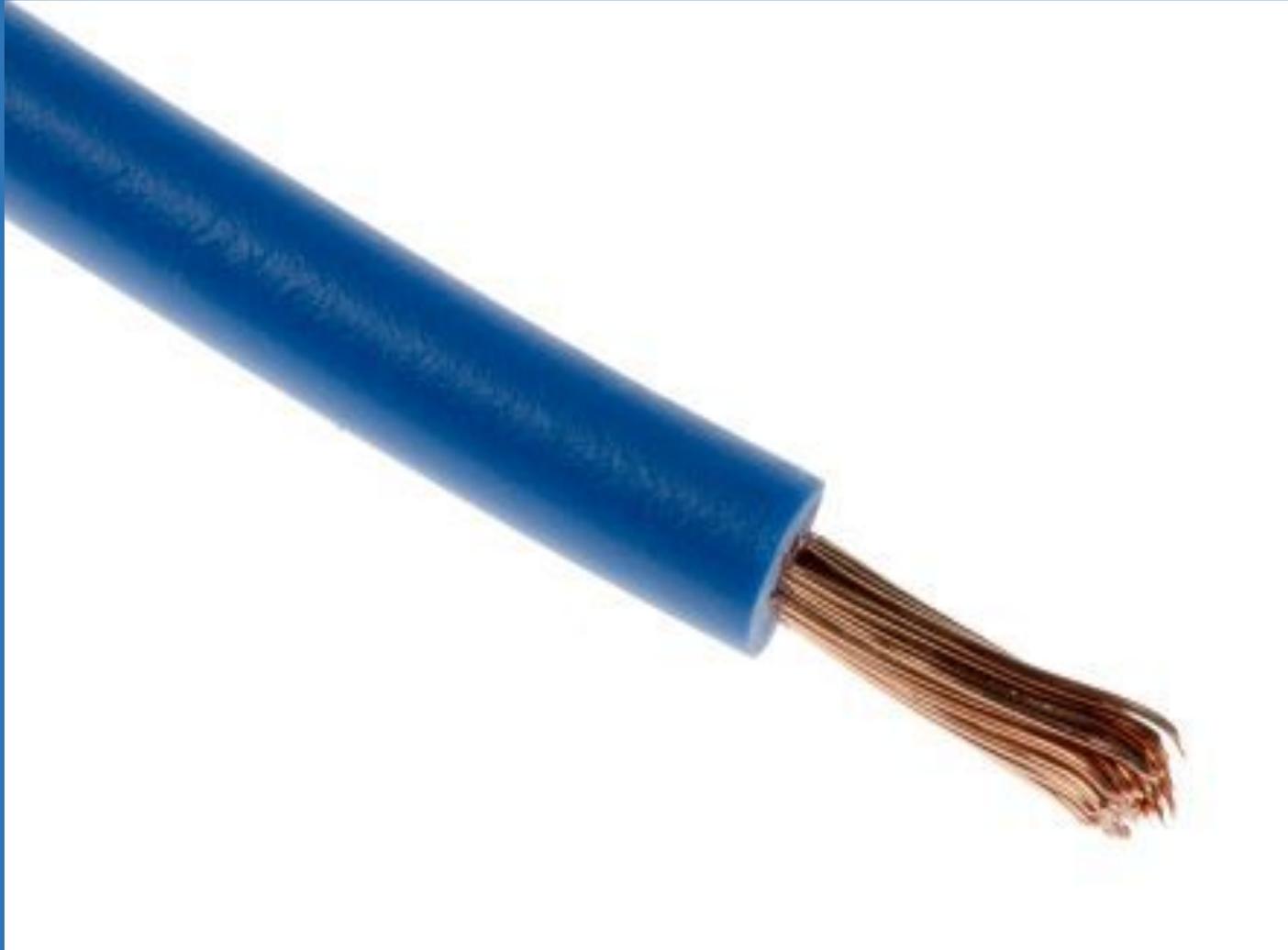


# What is its function?

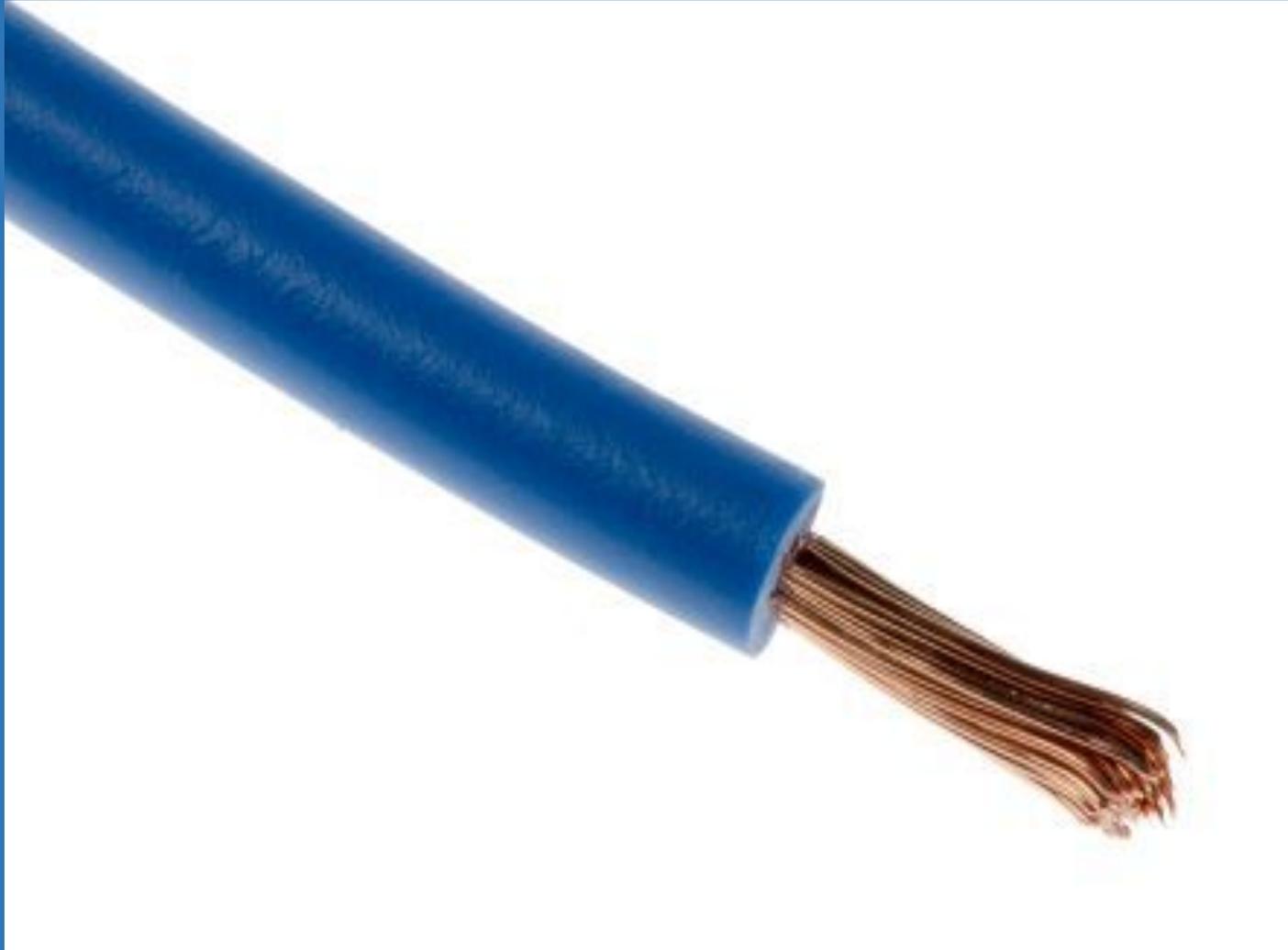

**It connects  
the  
components  
together.**



# Components (parts of a circuit)

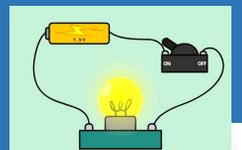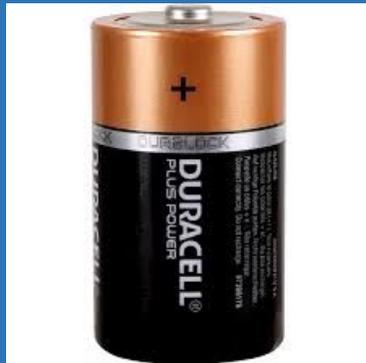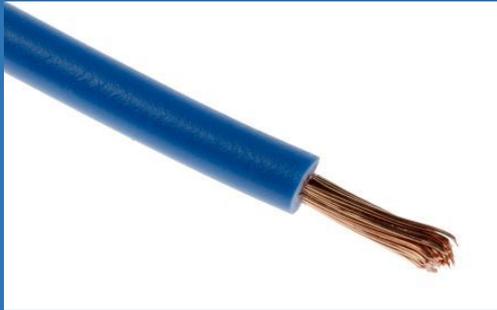

Time  
to  
think!

Will the light work?



Explain your answer.

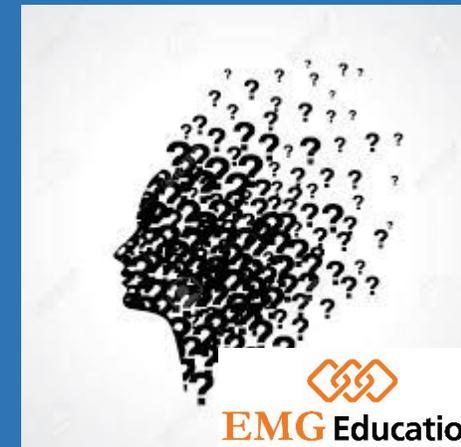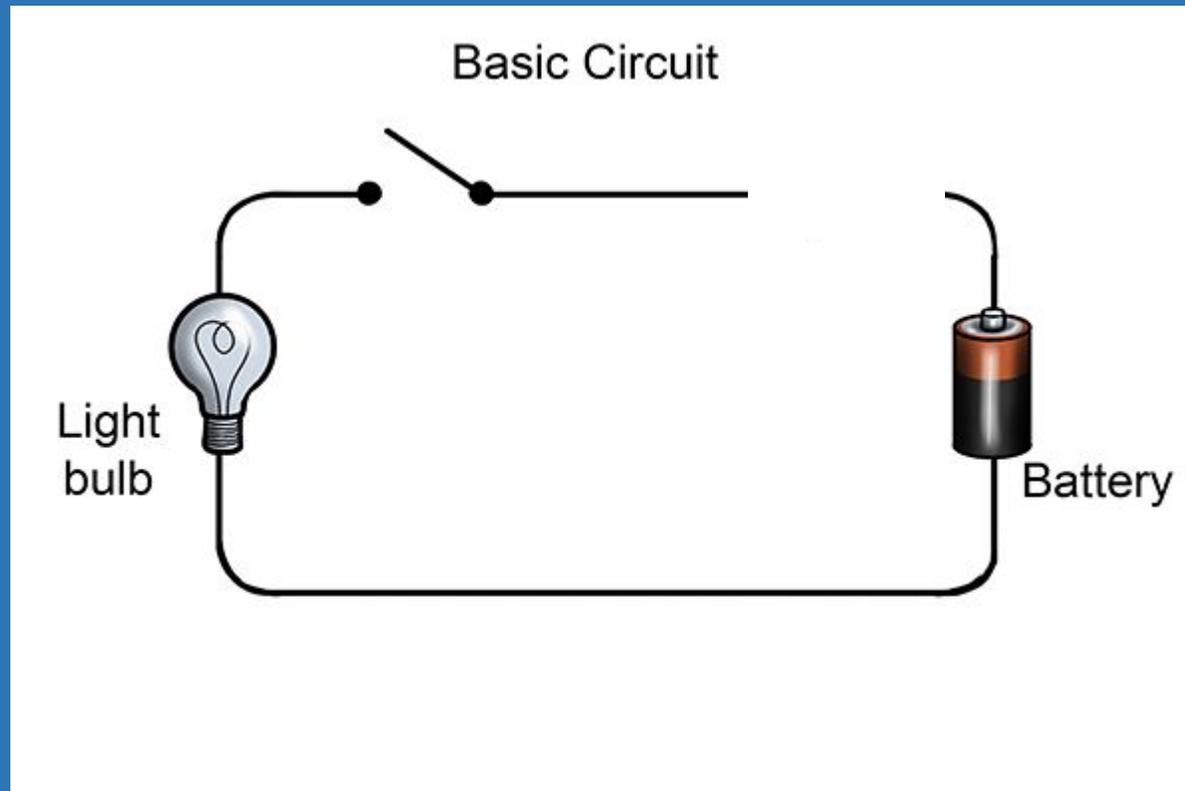

**It won't  
work!!!**

**Will the light work?**


**Explain your answer.**

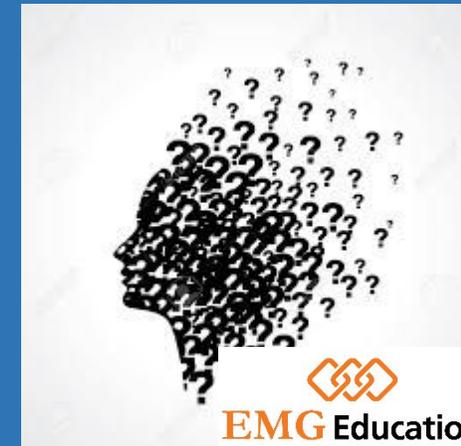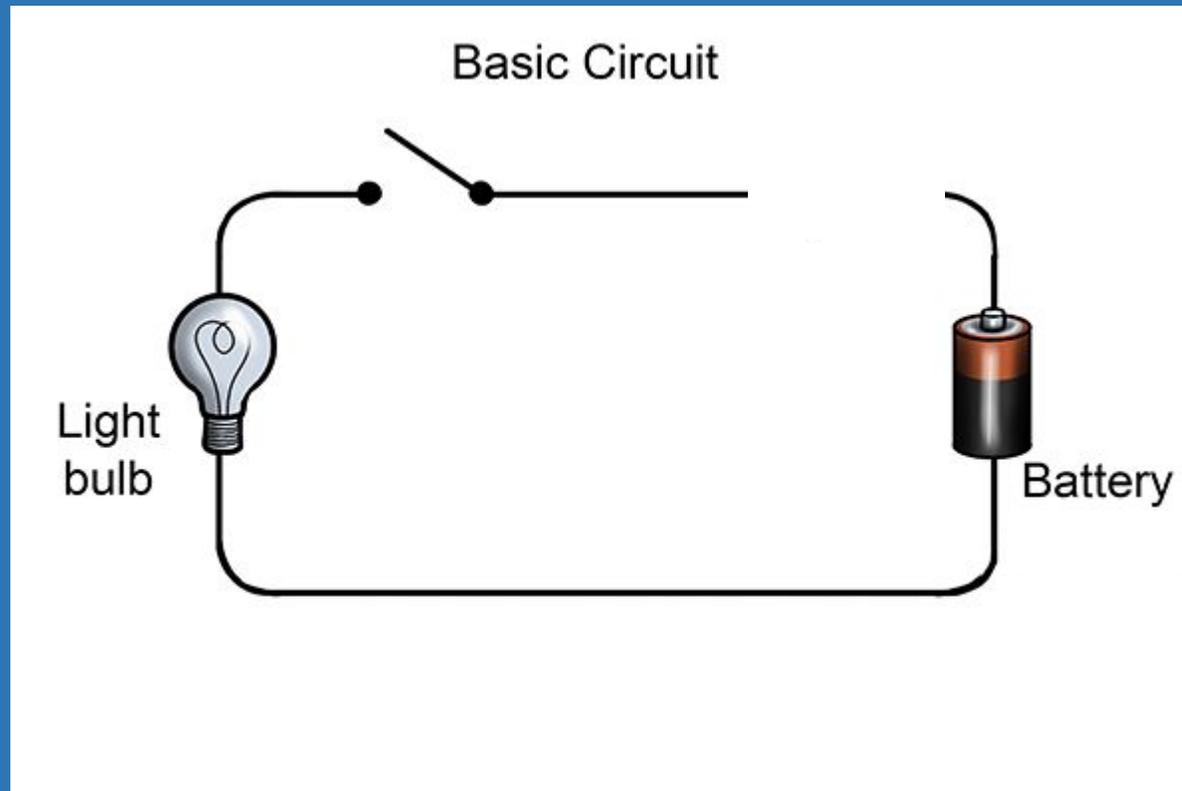

Time  
to  
think!

Will the light work?



Explain your answer.

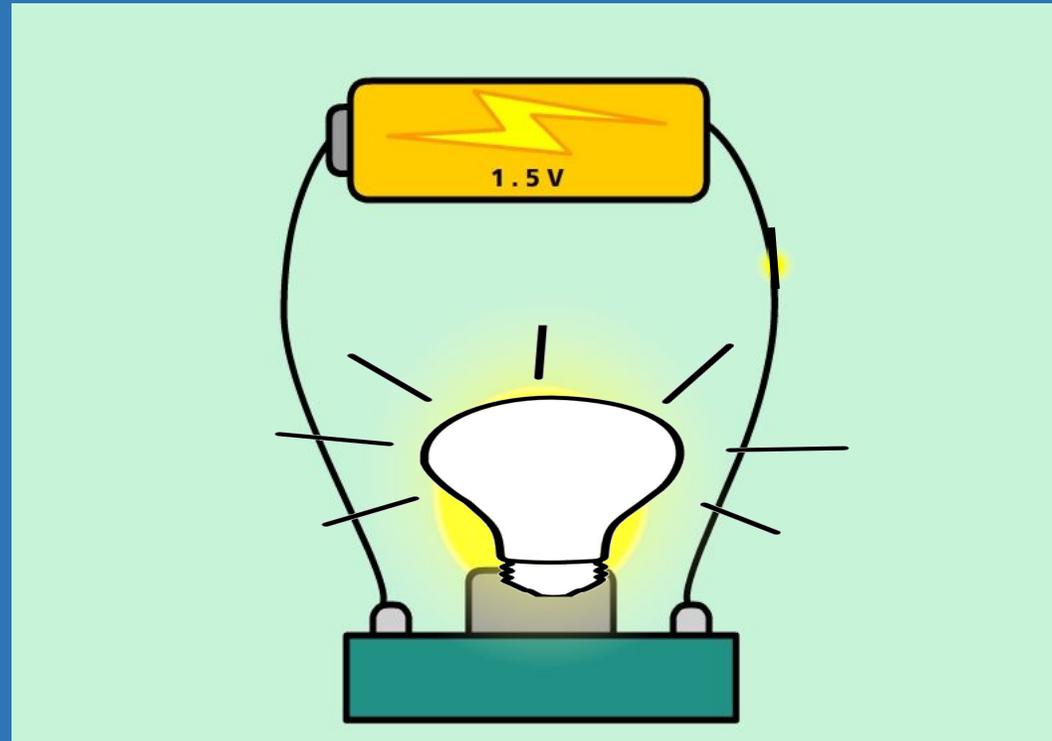

**It will  
work!**

**Will the light work?**



**Explain your answer.**

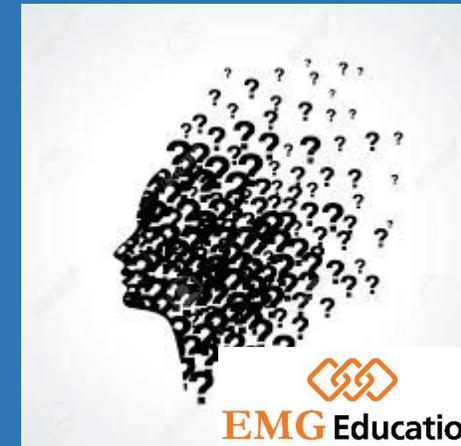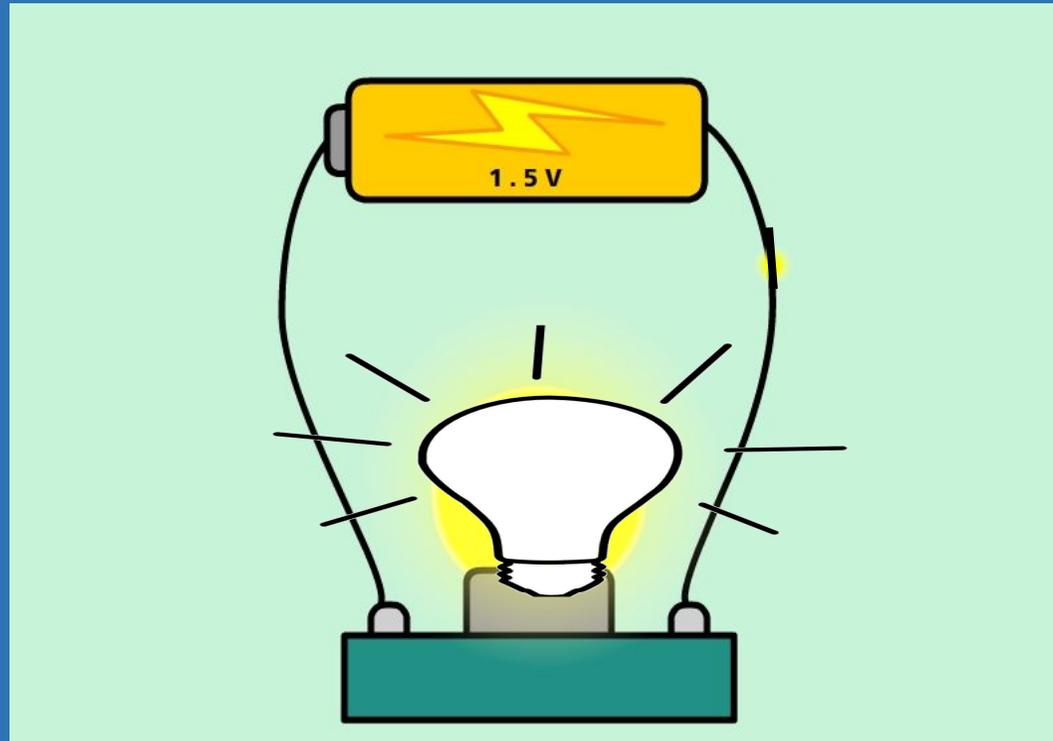

Time  
to  
think!

Will the light work?



Explain your answer.

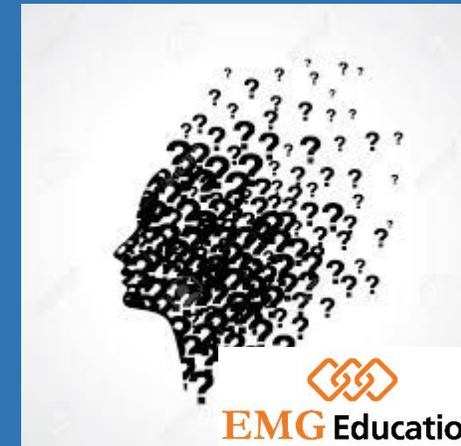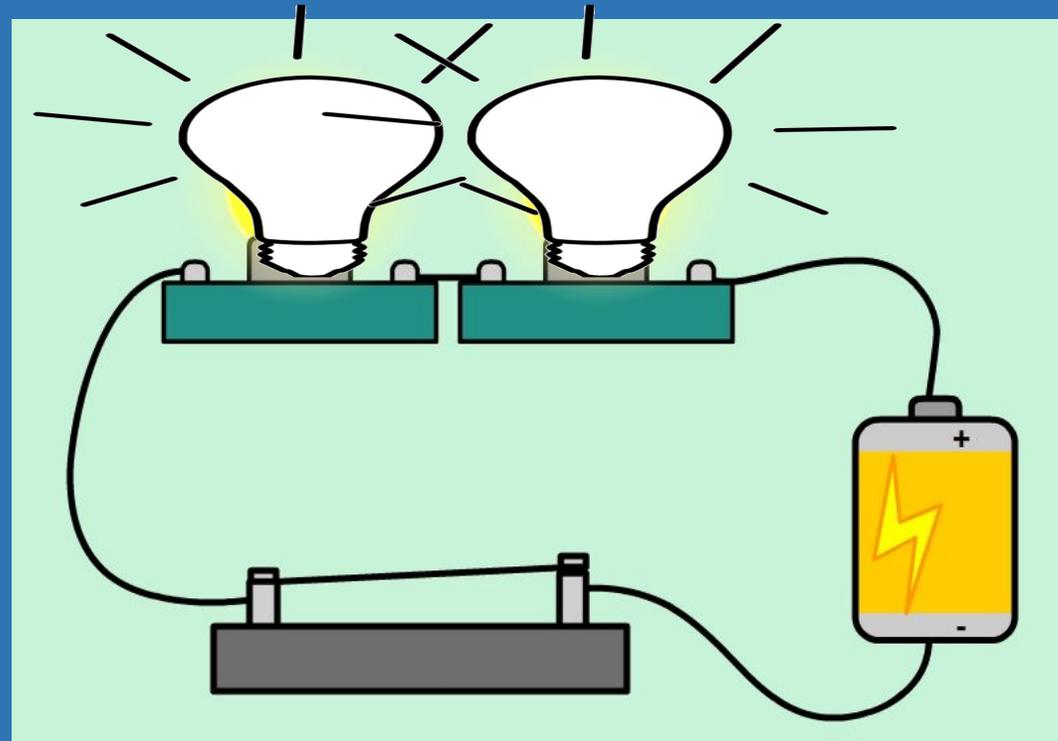

**It will  
work!**


**Will the light work?**

**Explain your answer.**

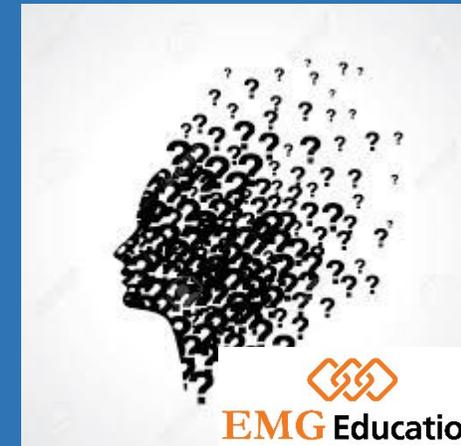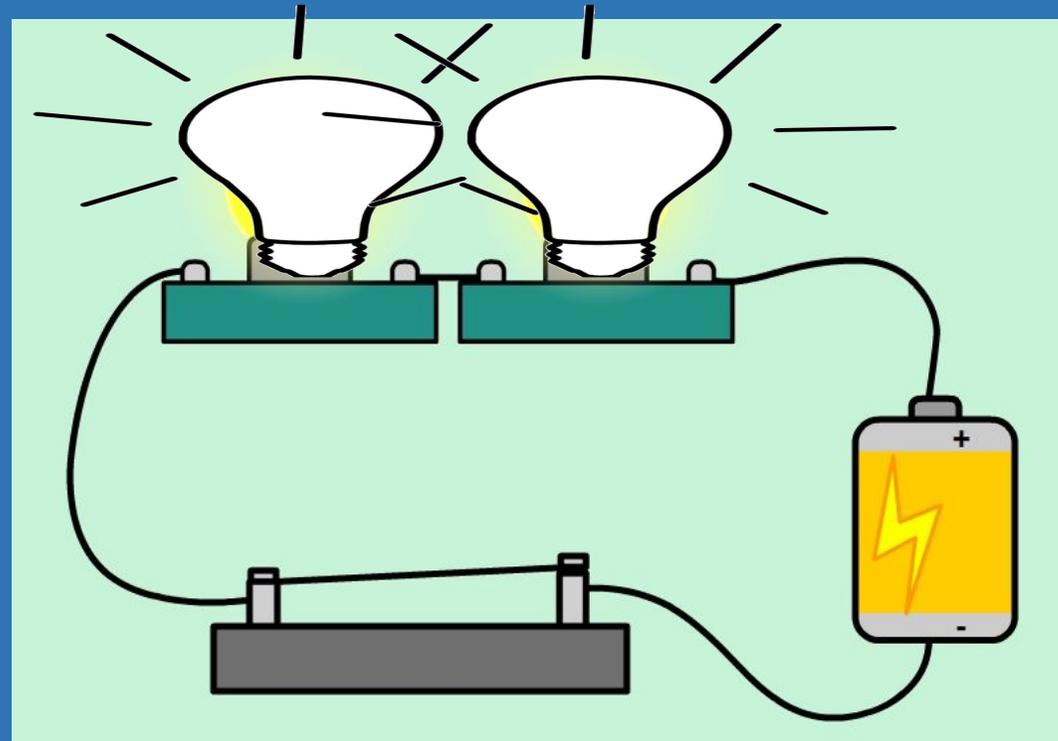
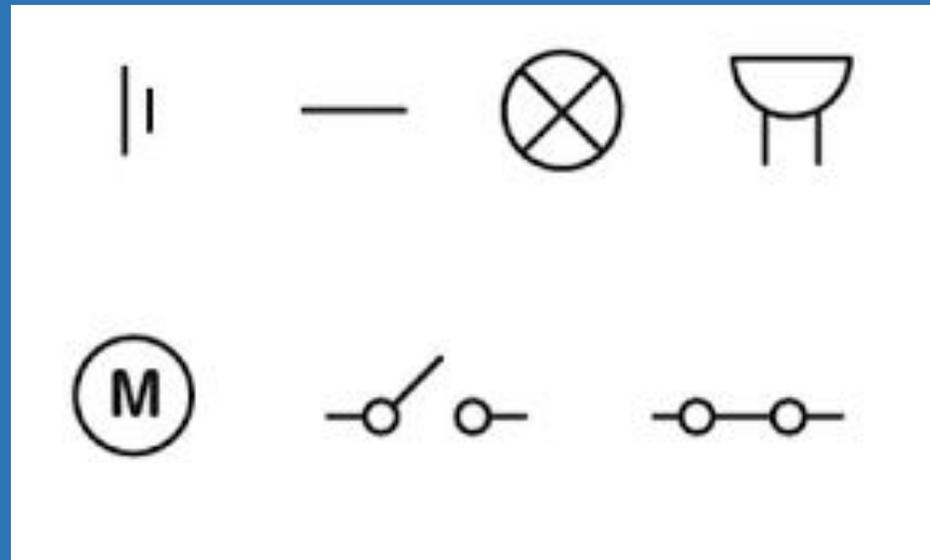
# Circuit Symbols

To make drawing circuits easier we use circuit symbols.




These are  
circuit  
symbols.

What is the symbol for a light?

Does anyone know?



# What is the symbol for a light?


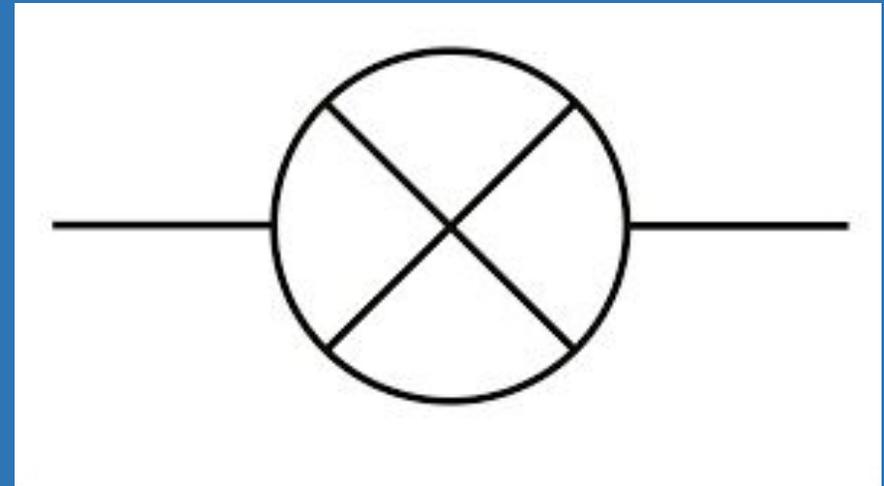


That's how we draw a light.

# What is the symbol for a battery?




# What is the symbol for a cell?

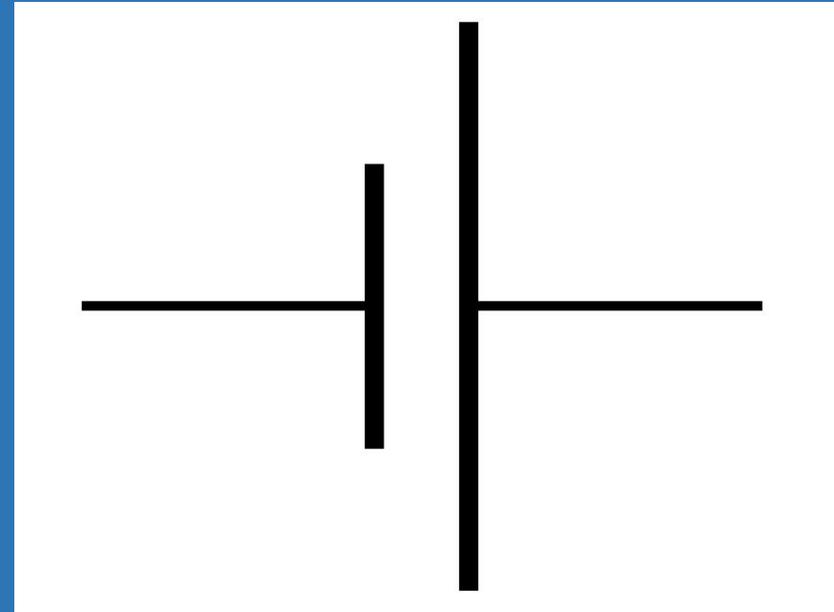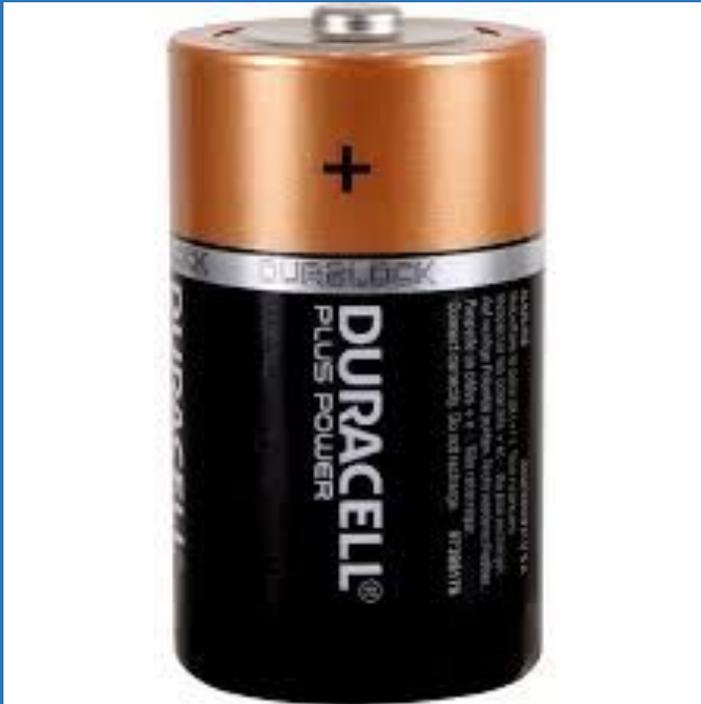

That's how we draw a cell.

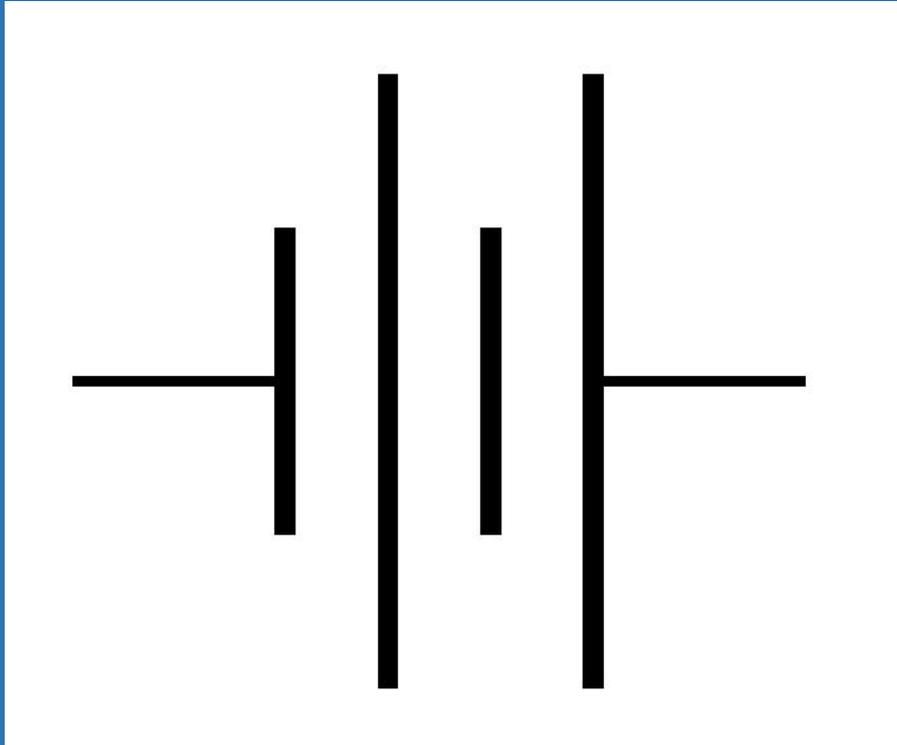
# Two batteries together looks like this....



What is the symbol for a **motor**?




What is the symbol for a **battery**?

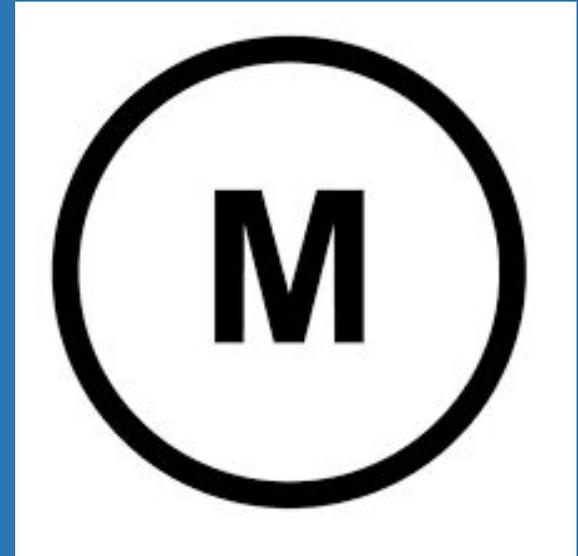

What is the symbol for a **switch**?




# What is the symbol for a **switch**?

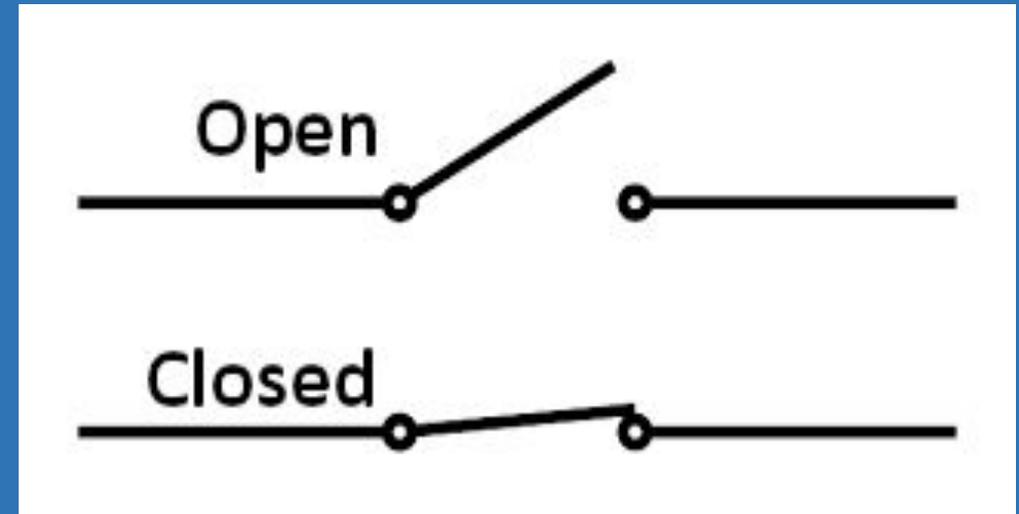




open switch

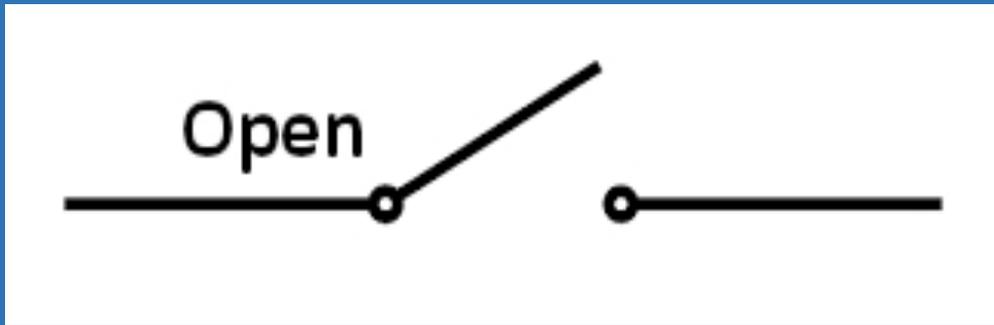

closed switch

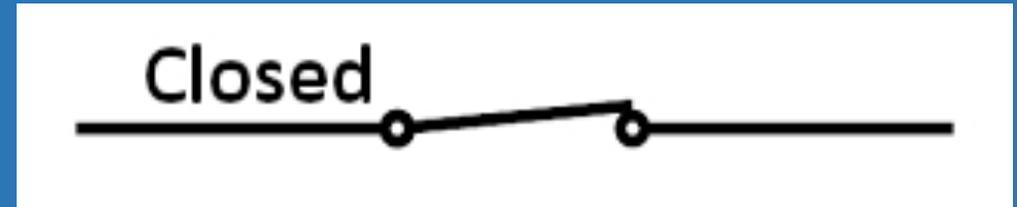


the circuit is off

the circuit is on


What is the symbol for a **buzzer**?





What is the symbol for a **buzzer**?

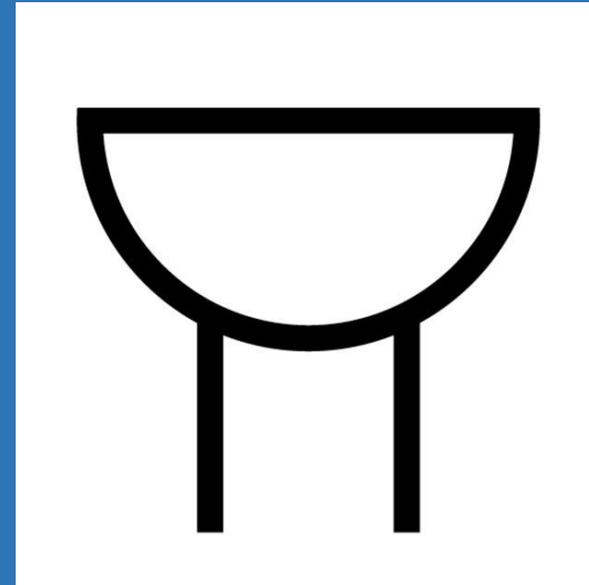


What is the symbol for a **wire**?

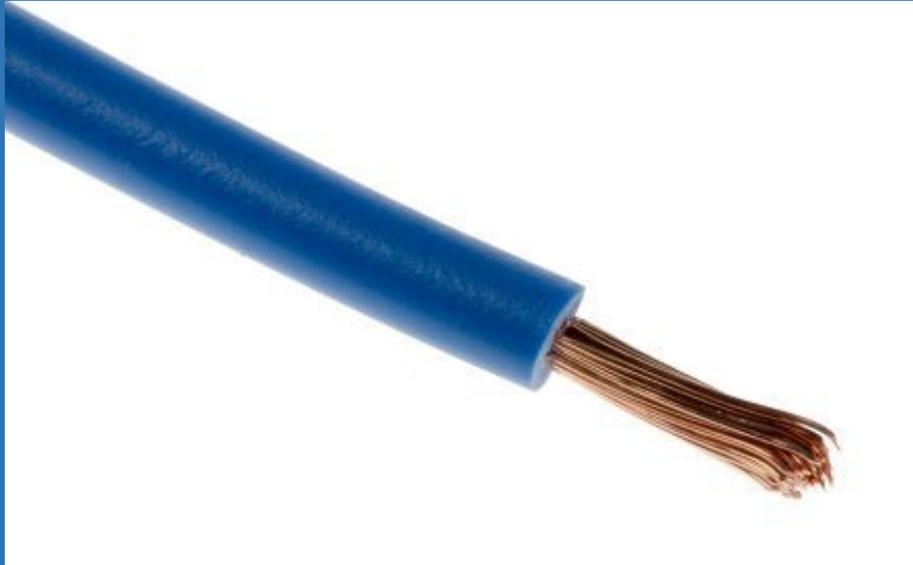


What is the symbol for a **wire**?

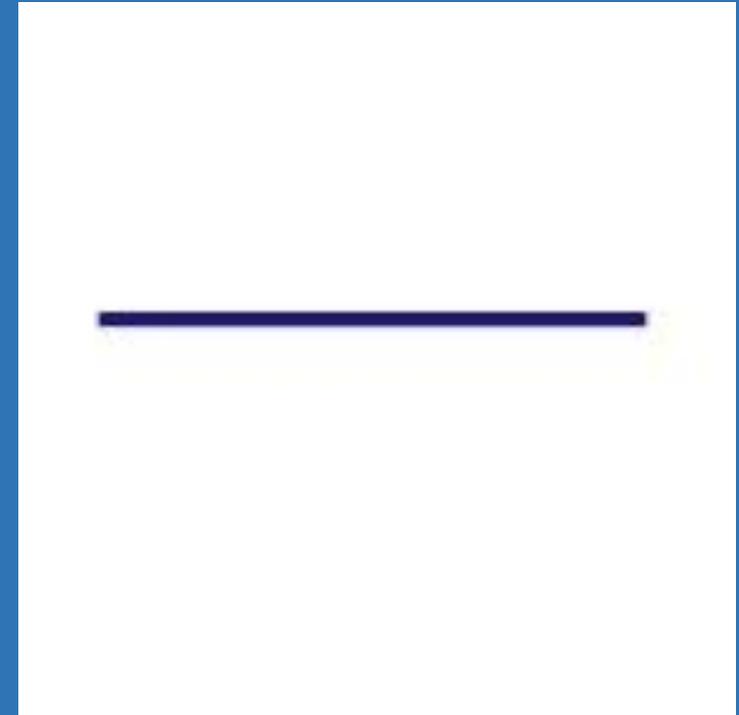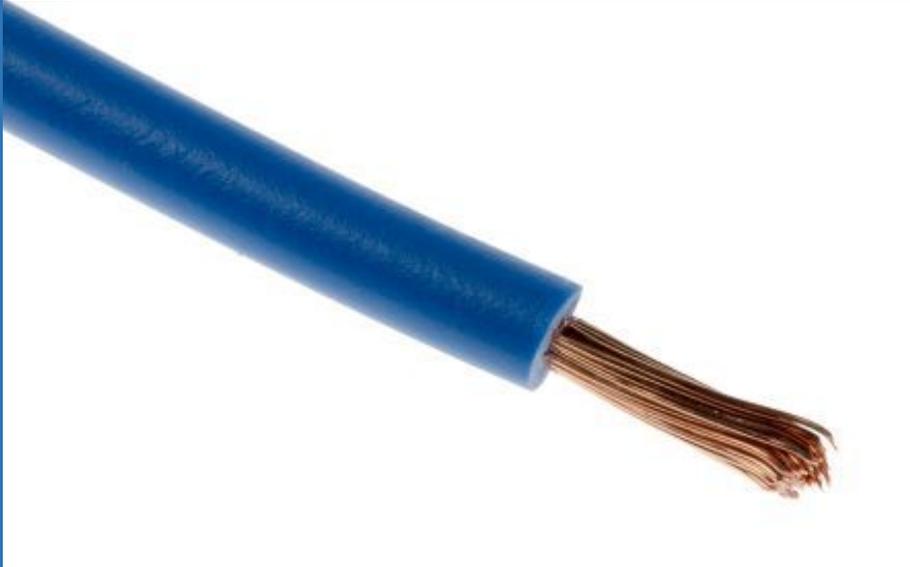

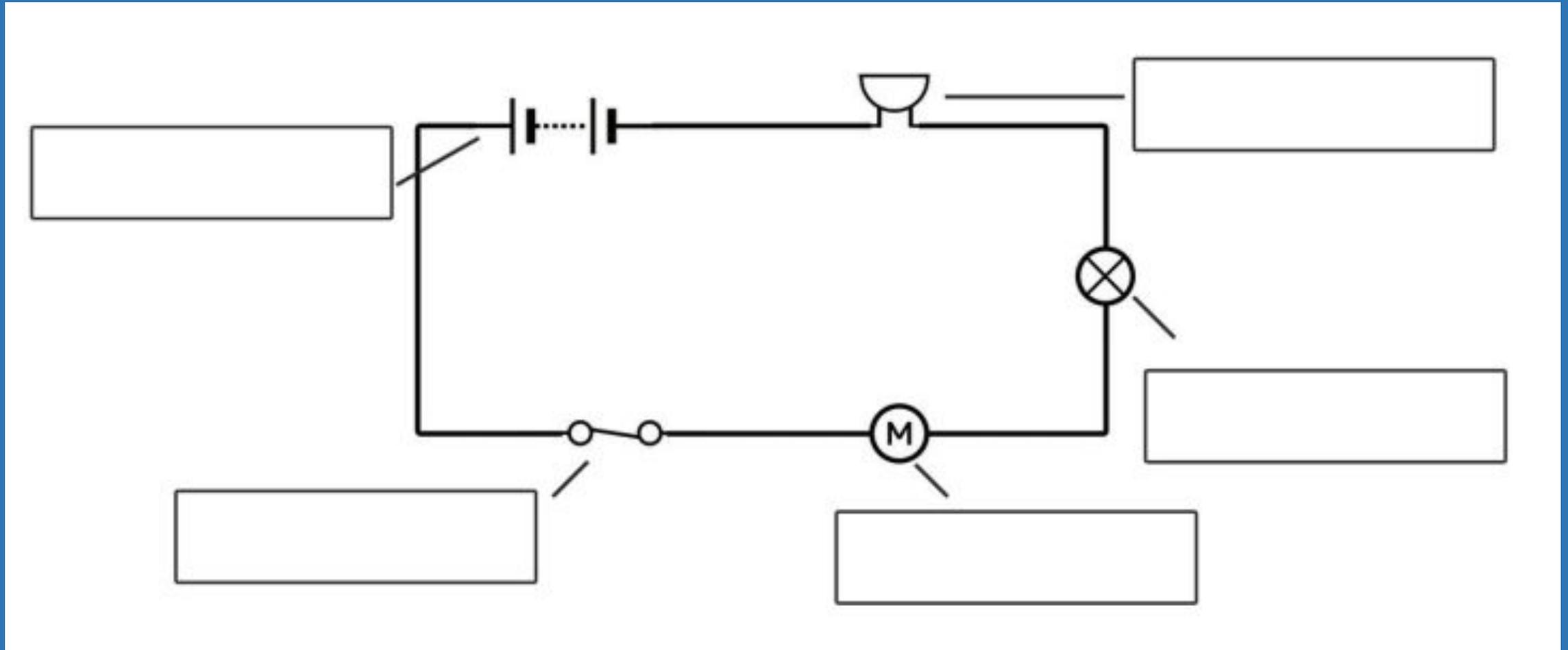Look at this circuit. **What are the components?**





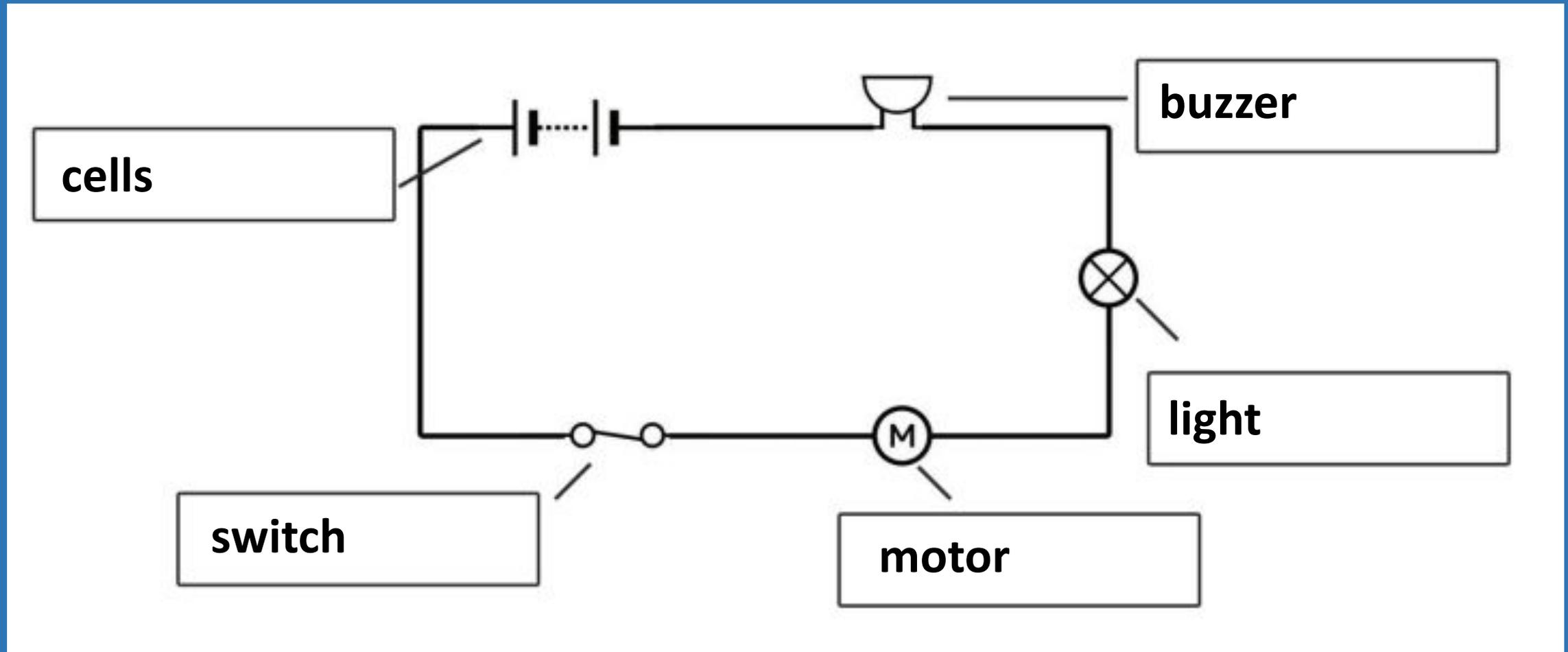Look at this circuit. **What are the components?**



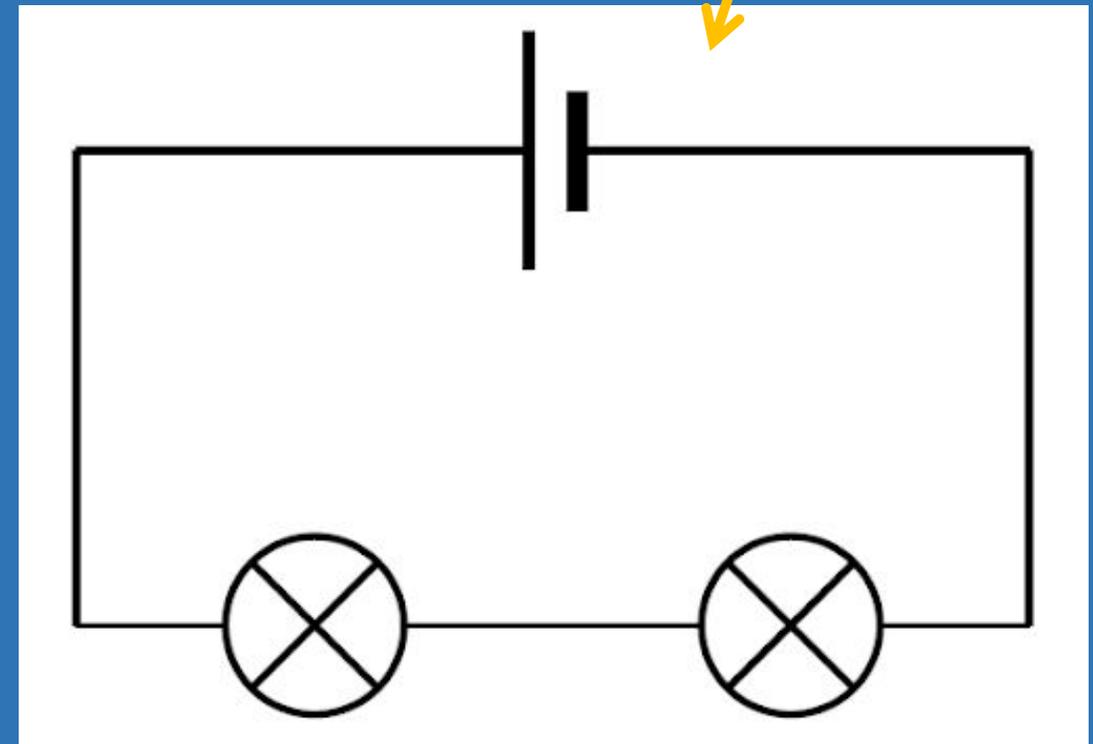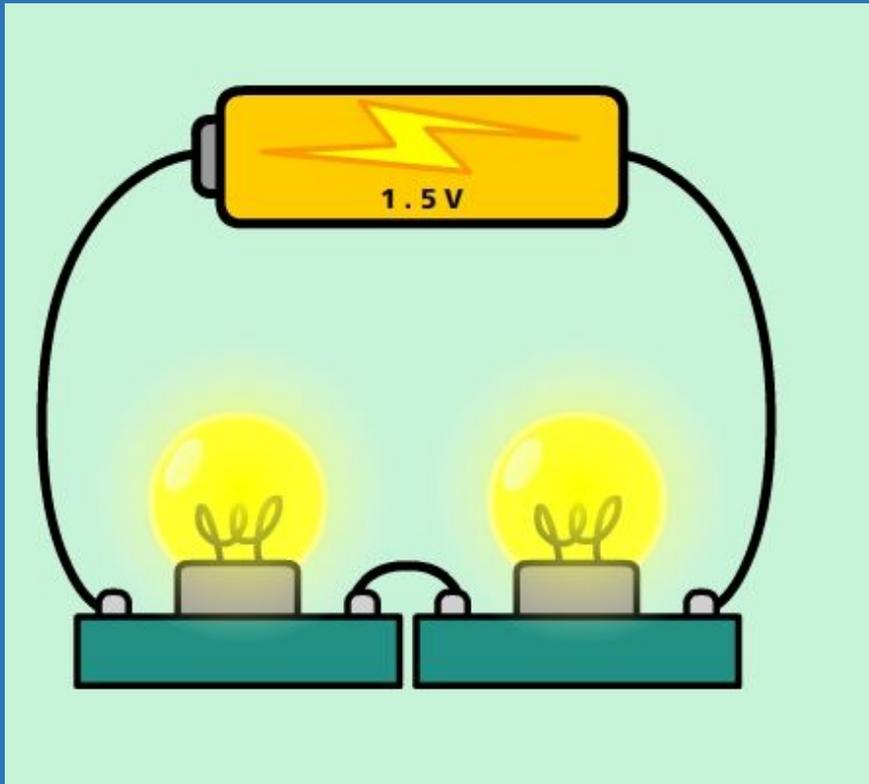
# Drawing a complete circuit

You need to draw  
circuit diagrams  
like this



# What components do you see?

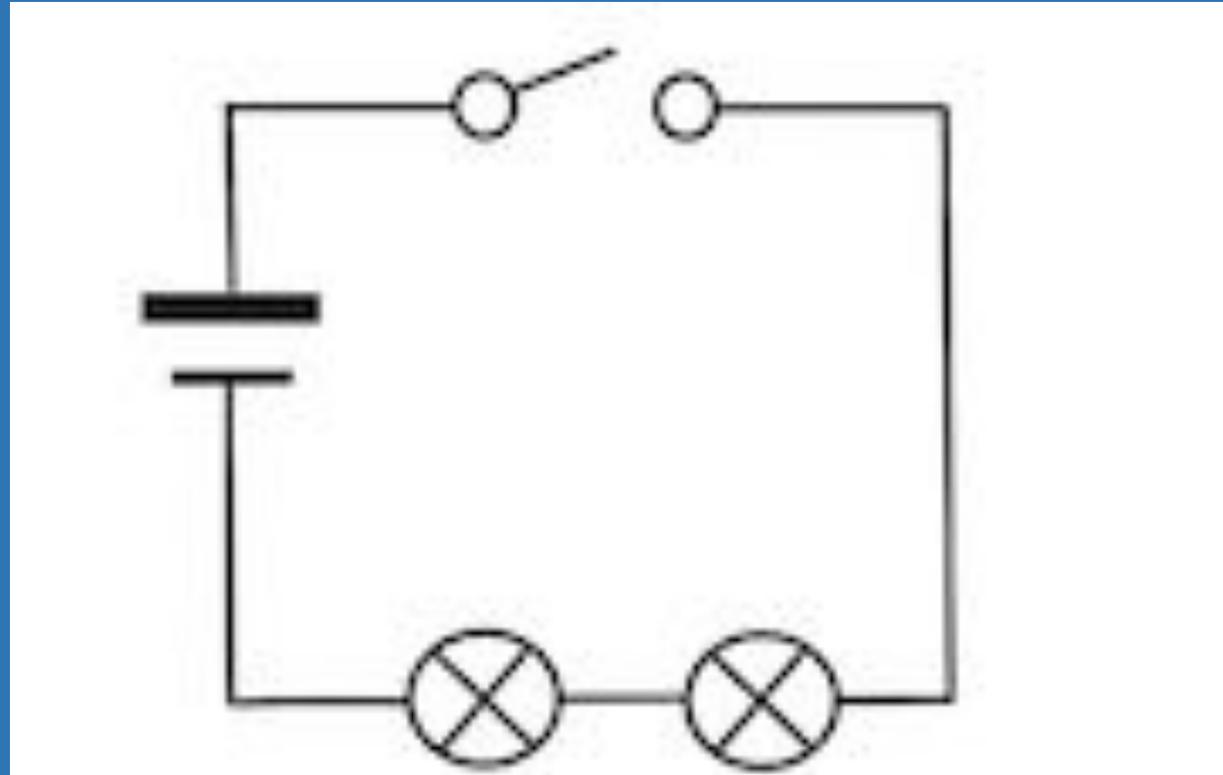


# What components do you see?

switch


cell

wire

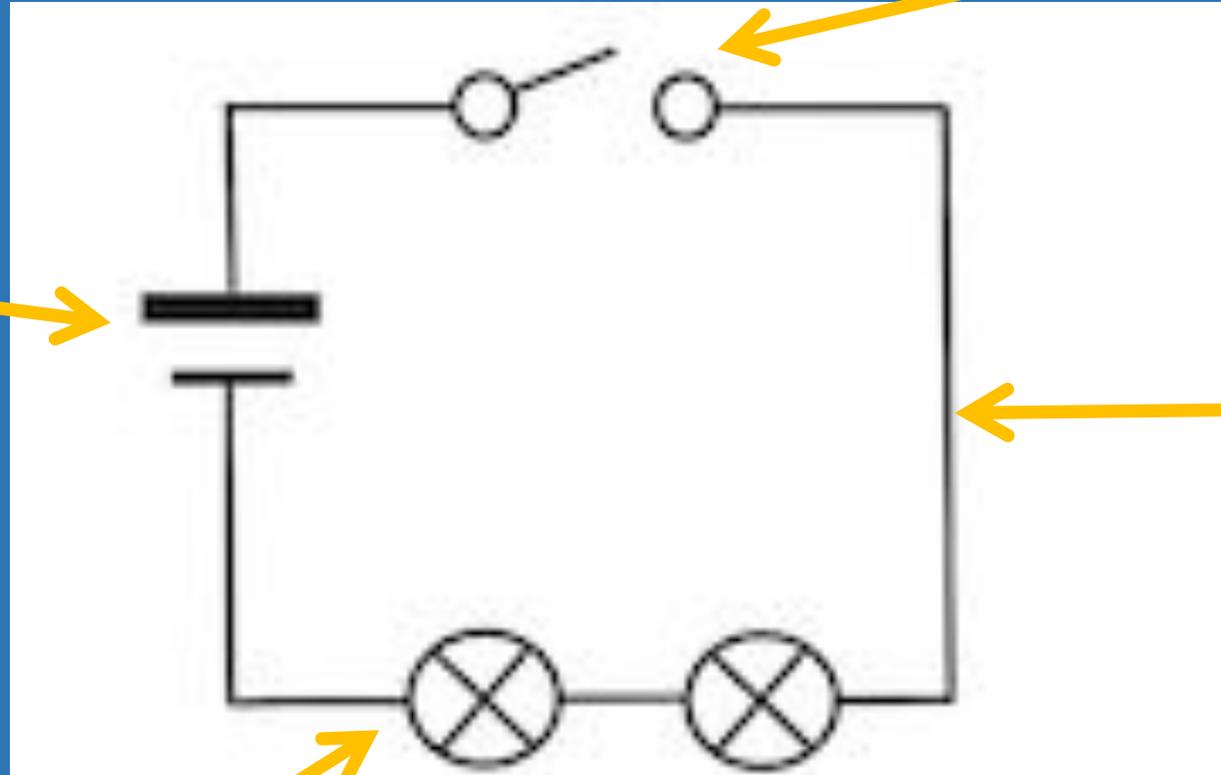

lamp


# What components do you see?

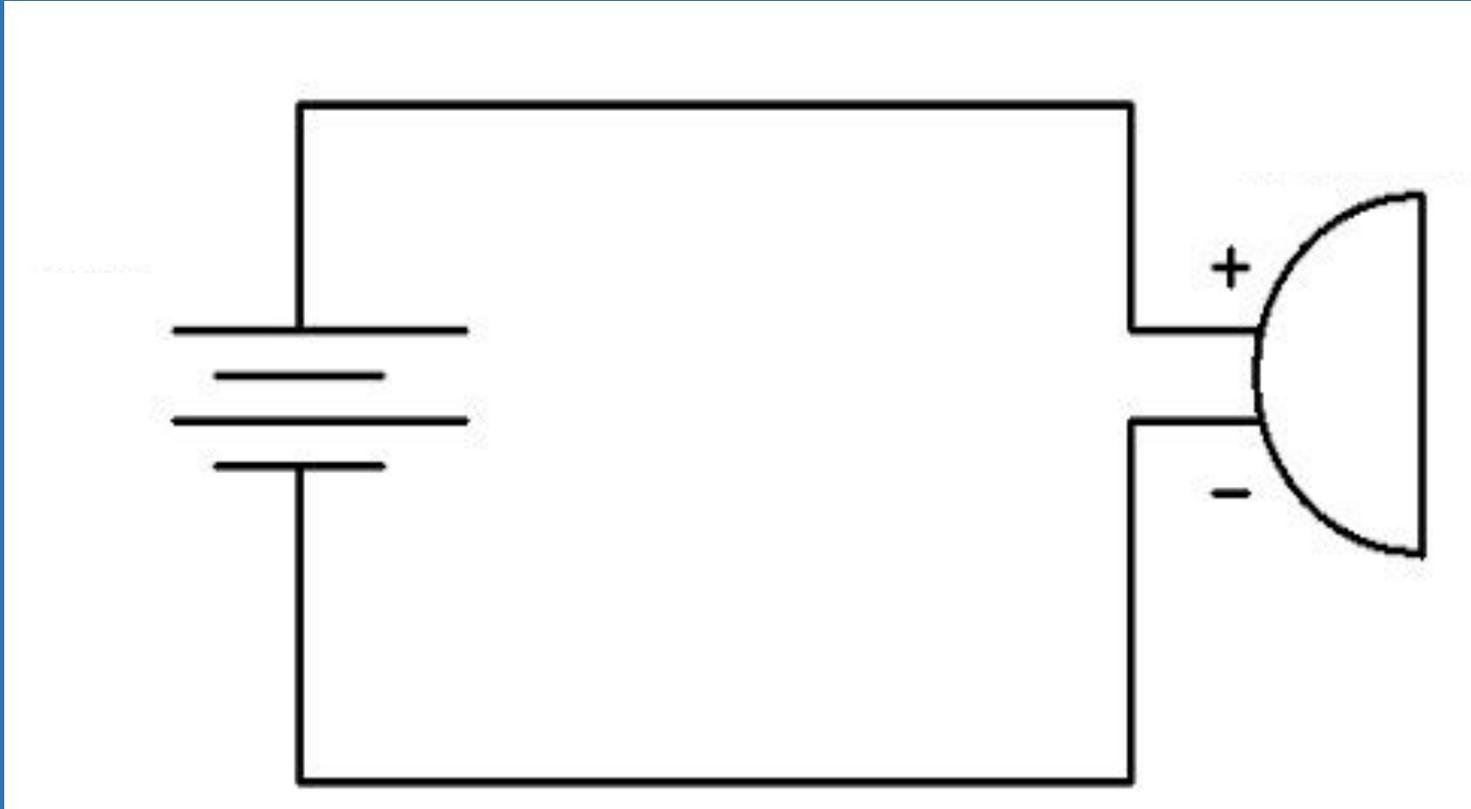

# What components do you see?

motor

cells

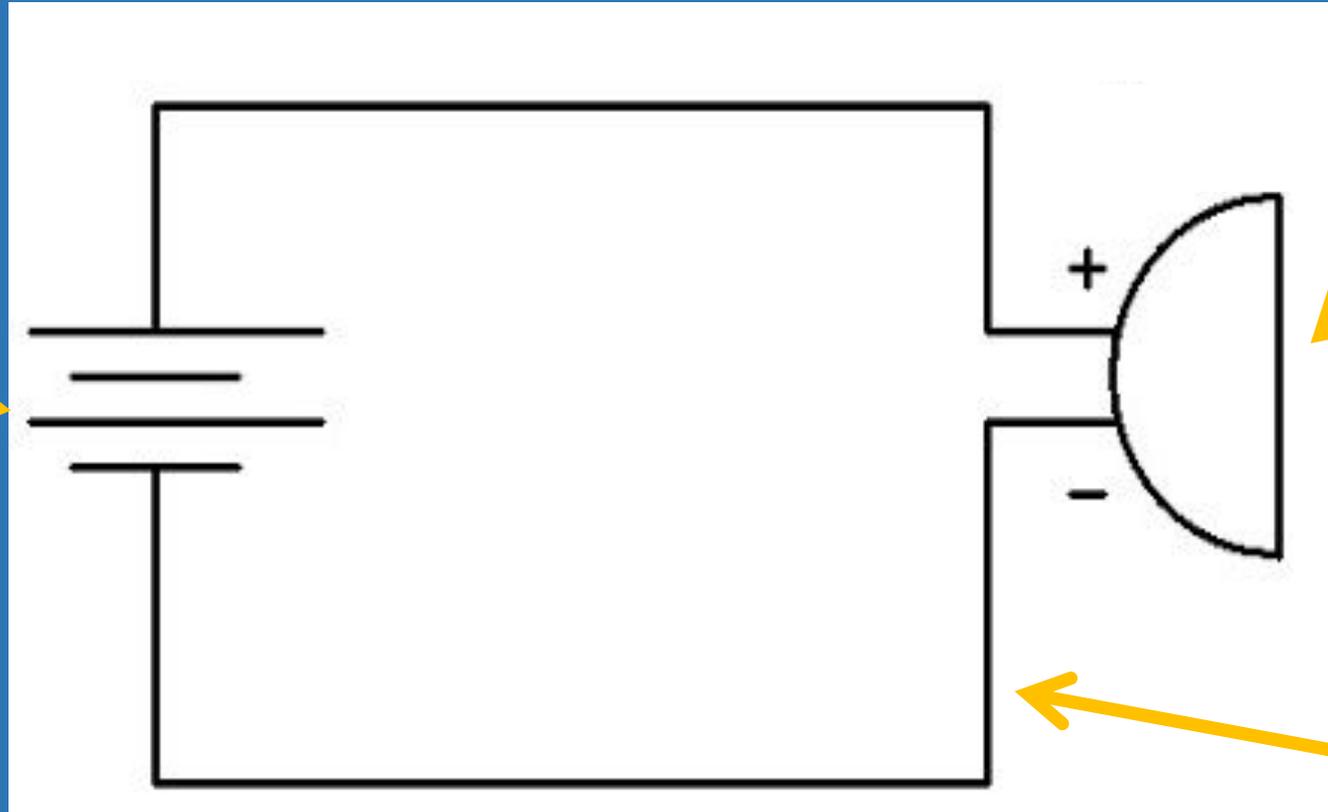

wire

# Today we have learned:

- parts of a circuit
- component functions
- circuit symbols
- how to draw circuits

